

PreLab6

Study the transition process of Circuits

Name

杨润霖

Score

Stu No.

2022533080

of 42

Part ONE Integrator

In Figure 1, the resistor $R=10\text{k}\Omega$, V_{in} is a square wave, $T=1\text{ms}$, 50% duty cycle, the high level of the square wave is 3V , the low level of the square wave is -3V .

1. Under what conditions does an RC circuit act as an integrator? ___1.5pt

$$V_{out} \ll V_{in}$$

$$t \ll RC$$

2. Calculate the capacitance of C @ $\tau=0.1T$, $\tau=T$, $\tau=10T$. ___3pt


$$\tau = 0.1T = 1 \times 10^{-4} = 10^{-4} \text{ s} \Rightarrow C = 1 \times 10^{-8} \text{ F}$$

$$\tau = T = 1 \times 10^{-3} = 10^{-3} \text{ s} \Rightarrow C = 1 \times 10^{-7} \text{ F}$$

$$\tau = 10T = 1 \times 10^{-2} = 10^{-2} \text{ s} \Rightarrow C = 1 \times 10^{-6} \text{ F}$$

3. Simulate the four circuits using MultiSim

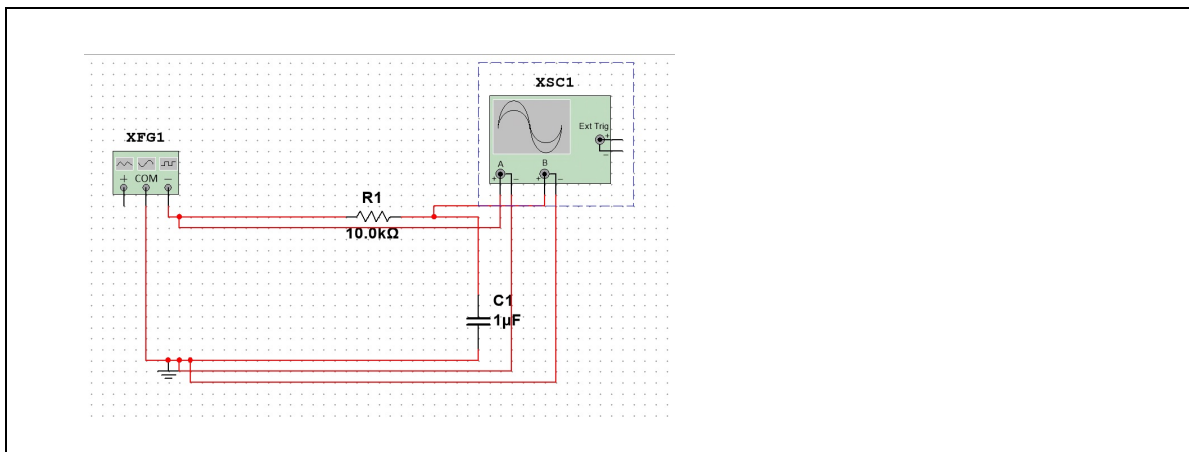- (1) take a screenshot of the circuit schematic (one case is ok). ___2pt



- (2) take screenshots of the output voltage waveform (at least two cycles) @ $\tau=0.1T$, $\tau=T$, $\tau=10T$ ___3pt



Part TWO Differentiator

In Figure 2, the resistor $R=10\text{k}\Omega$, V_{in} is a square wave, $T=1\text{ms}$, 50% duty cycle, the high level of the square wave is 3V , the low level of the square wave is -3V .

1. Under what conditions does an RC circuit act as a differentiator? ___ 1.5pt

$$V_{in} \gg V_{out}$$

$$t \gg RC$$


2. Calculate the capacitance of C @ $\tau = 5T$, $\tau = 0.1T$. ___ 2pt

$$\tau = 5T = 5 \times 10^{-3} = 10^{-2} \text{ s} \Rightarrow C = 5 \times 10^{-7} \text{ F}$$


$$\tau = 0.1T = 10^{-4} = 10^{-4} \text{ s} \Rightarrow C = 10^{-8} \text{ F}$$

3. Simulate the two cases using MultiSim.

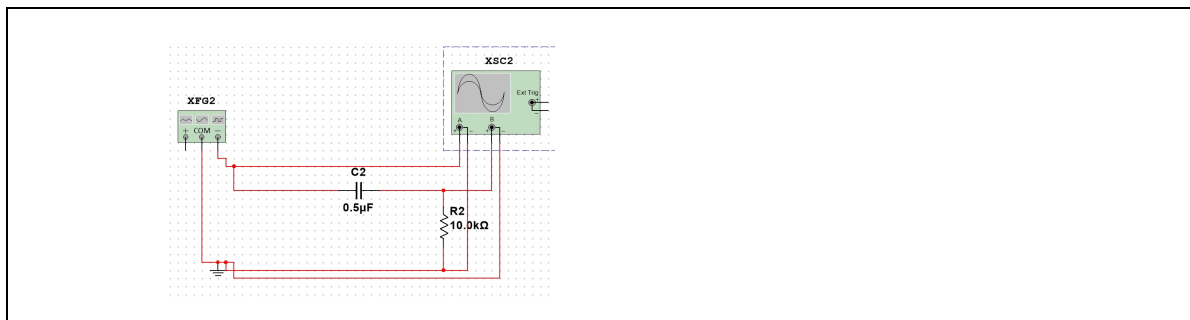- (1) Take a screenshot of the circuit schematic (one case is ok). ___ 1.5pt



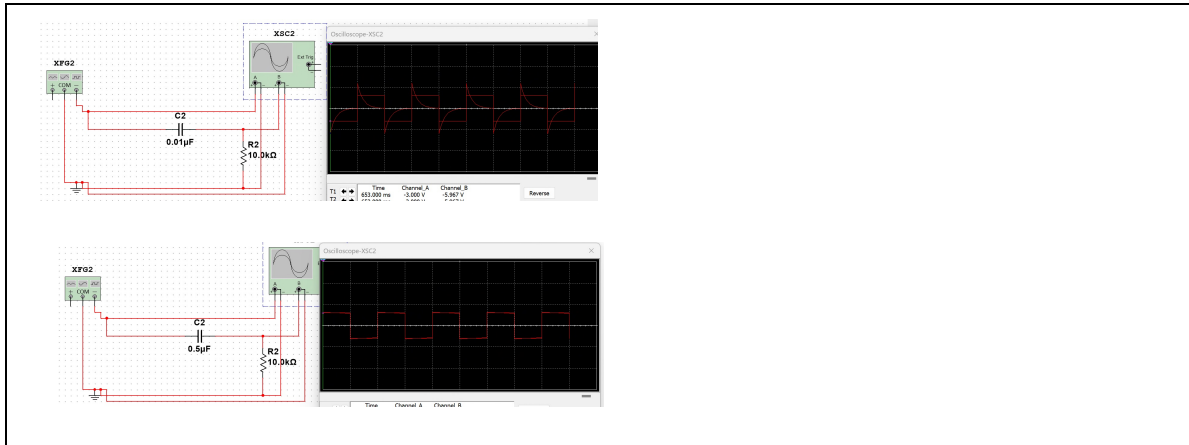- (2) Take screenshots of the input and output voltage waveform (at least two cycles) @ $\tau=5T$, $\tau=0.1T$ respectively (input and output are in the same coordinate). ___4pt



Part THREE RLC Circuit

In the RLC series circuit shown in Figure 3, $L=0.5\text{H}$, $C=0.1\mu\text{F}$. V_{in} is a square wave, $T=10\text{ms}$, 50% duty cycle, the high level of the square wave is 3V, the low level of the square wave is -3V.

1. Is the circuit overdamped, underdamped or critically damped? Why? ___6pt

① $R=1.3\text{k}\Omega$

$$\alpha = \frac{R}{2L} = \frac{1.3\text{k}}{2 \times 0.5} = 1.3\text{k} \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.5 \times 0.1 \times 10^{-6}}} = 4.5\text{k} \quad \alpha < \omega_0$$


Underdamped

② $R=6.2\text{k}\Omega$

$$\alpha = \frac{R}{2L} = 6.2\text{k} \quad \omega_0 = \frac{1}{\sqrt{LC}} = 4.5\text{k} \quad \alpha > \omega_0$$


Overdamped

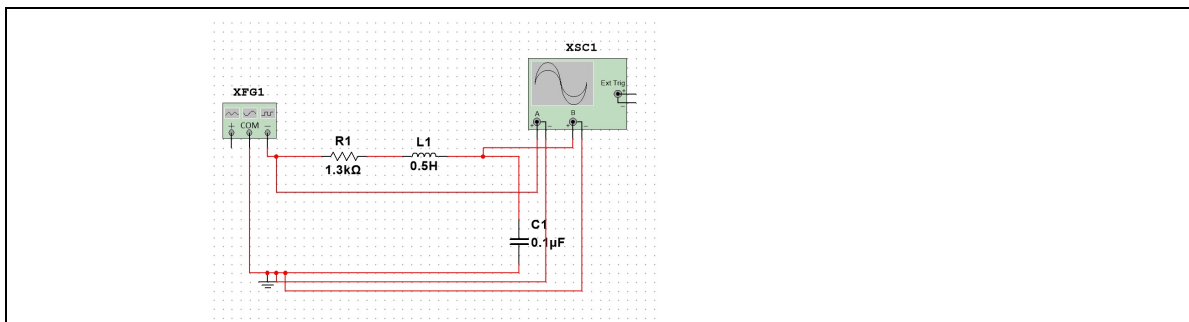2. Simulate the RLC series circuit using MultiSim. Take a screenshot of the circuit schematic when $R=1.3\text{k}\Omega$. ___1pt




3. Take a screenshot of the input and output transient voltage waveform (input and output are in the same coordinate). 6pt

$R=1.3k\Omega$

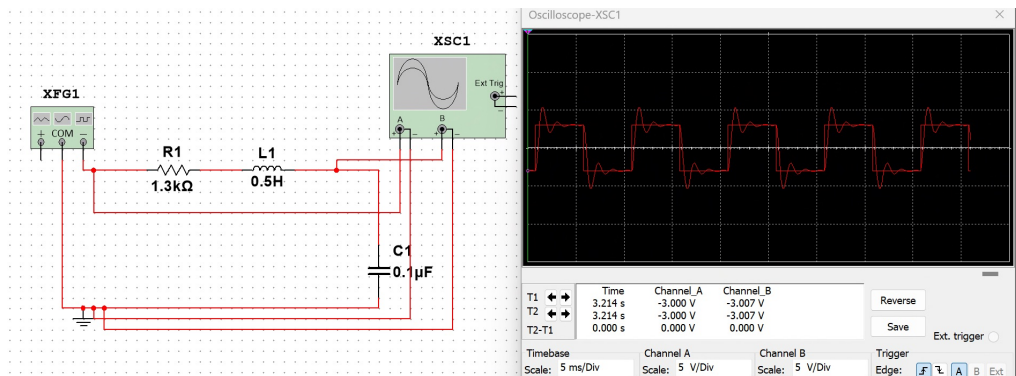


$R=6.2k\Omega$

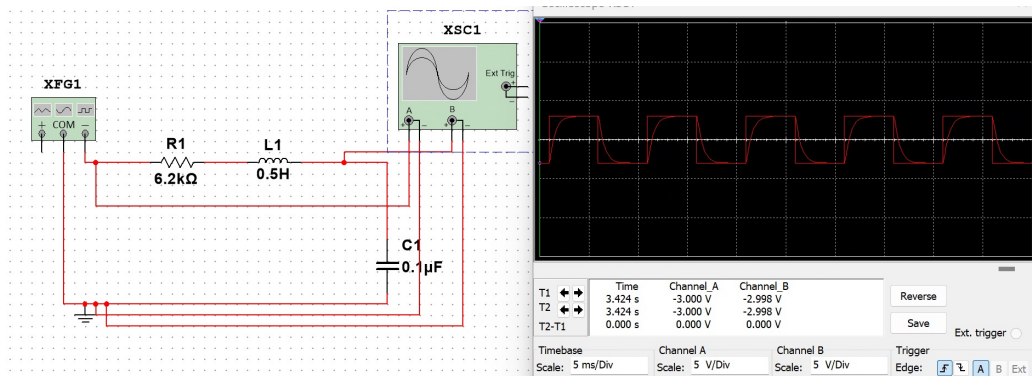

4. Record the necessary data, and get decay constant $[s^{-1}]$ α and the resonant frequency. 6pt

$R=1.3k\Omega$

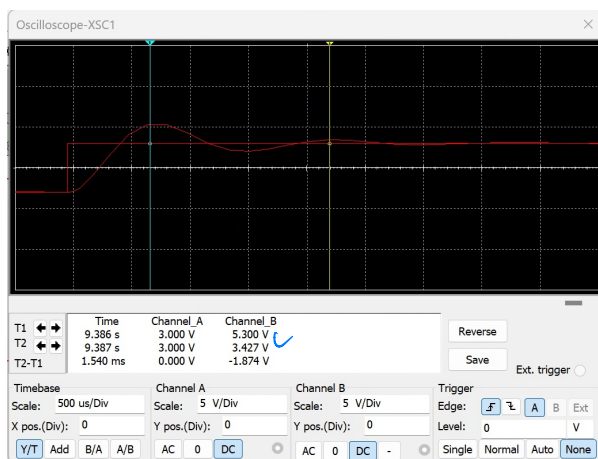

$$T = 1.540 \text{ ms} = 1.54 \times 10^{-3} \text{ s} = \frac{2\pi}{\omega_0}$$

$$\Rightarrow \omega_0 = \frac{2\pi}{T} = 4079.99 \text{ rad/s}$$

$$U_1 = 5.3 - 3 = 2.3 \text{ V} \quad U_2 = 3.427 - 3 = 0.427$$

$$\alpha = \frac{1}{T} \ln \frac{U_1}{U_2} = 1093.43$$