

# Lab3 Report

Name 杨润康 TA Checkoff \_\_\_\_\_

Teammate 赵汉卿 Score          /63

## Part One: Superposition Theorem

- Consider the circuit given in Fig. 1. that you have analyzed in Prelab, in which  $R_L$  is  $10\text{k}\Omega$ . Check the values of the resistors using the multimeter. Record the values in Table2. \_\_\_/4pt

Table 1.

Resistor	Nominal Value	Ohmmeter Reading
R1	$2.2\text{k}\Omega$	$2.190\text{k}\Omega$
R2	$1.5\text{k}\Omega$	$1.497\text{k}\Omega$
R3	$1.0\text{k}\Omega$	$1.008\text{k}\Omega$
$R_L$	$10\text{k}\Omega$	$10.03\text{k}\Omega$

- Construct the circuit (Fig. 1) that you have analyzed in Prelab on your protoboard and to to verify superposition.

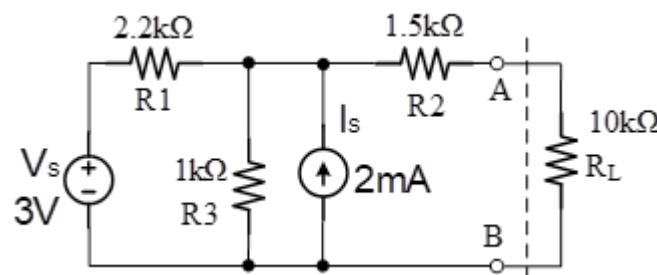


Fig. 1

- When  $V_S$  acting alone, measure  $U_L'$  and  $I_L'$ .
- When  $I_S$  acting alone, measure  $U_L''$  and  $I_L''$ .
- Superposition ( $V_S$  acting alone +  $I_S$  acting alone)
- Record the results in Table 2 \_\_\_/12pt

$$\%Error = \frac{|Experiment Value - Theory Value|}{Theory} \times 100\%$$

Table 2

	$U_L$ (V)	$U_L'$ (V)	$U_L''$ (V)	$I_L$ (mA)	$I_L'$ (mA)	$I_L''$ (mA)
Theory	1.90	0.769	1.13	$190 \times 10^{-3}$	$76.9 \times 10^{-3}$	$113 \times 10^{-3}$
Experiment	1.989	0.773	1.124	$200.0 \times 10^{-3}$	$77.0 \times 10^{-3}$	$117 \times 10^{-3}$
%Error	4.7%	0.52%	0.53%	5.2%	0.13%	3.5%

3. Comment on the results found in Table2. \_\_/8pt

The theoretical value and experimental value are very close to each other (the error is small and the error occurred since the sources are not ideal)  
Both show that in a linear circuit with several sources, the voltage and current responses in any branch is the algebraic sum of the voltage and current responses due to each source acting independently with all other sources replaced by their internal impedance. (The superposition theorem is true)

## Part Two: Thevenin's Theorem and Norton's Theorem

- Construct the circuit (Fig. 2) that you have analyzed in Preliminary Work on your Breadboard and to verify superposition.

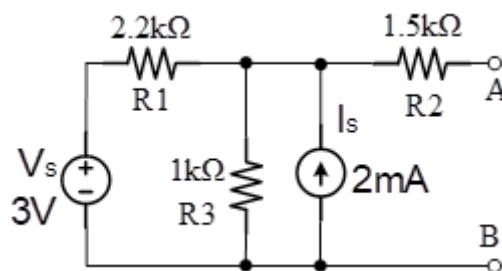


Fig. 2



- Measure the open circuit voltage  $U_{oc}$
- Measure the short circuit current  $I_{sc}$ . This is accomplished by placing an Ammeter between A and B. In this manner, the Ammeter will act as a short circuit.
- Record the results in Table 3. \_\_/9pt

直接抄预习报告

Table 3

	$U_{oc}$ /V	$I_{sc}$ /mA	$R_0$ /kΩ
Theory	2.31	1.06	2.18
Experiment	2.435	1.066	2.228
%Error	5.4%	0.57%	2.2%

5. Draw the Thévenin's and Norton's equivalent circuit obtained **experimentally**. \_\_\_/8pt

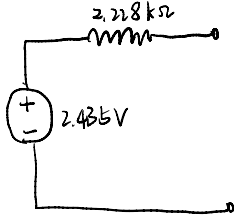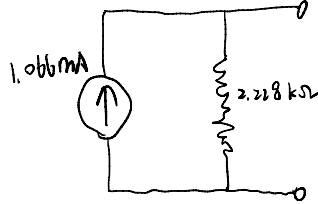Thévenin Equivalent Circuit	Norton Equivalent Circuit
	

6. Validate Thévenin theorem.

- 1) Connected the variable resistor  $R_L$  between terminals A and B of the two-terminal active network (Fig. 3), change the resistance of  $R_L$  and measure the external characteristics of the linear two-terminal active network

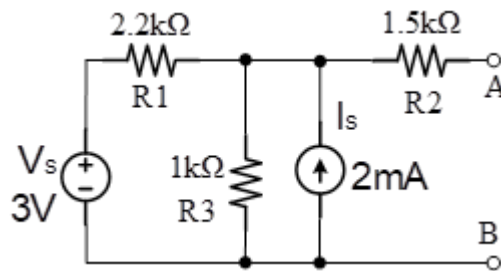


Fig. 3

- 2) Connected the variable resistor  $R_L$  as the load of the Thévenin Equivalent Circuit, change the resistance of  $R_L$  and measure the external characteristics of the Thévenin Equivalent Circuit.
- 3) Compare the external characteristics of 1) and 2) and validate Thévenin theorem.
- 4) Record the corresponding voltages and currents into the Table 4. \_\_\_/10pt

Table 4.


$R_L/\Omega$	0	2k	$R_0$	6k	$\infty$
$V_{load}/V$ original two-terminal network, experiment	0	1.166	1.230	1.797	2.448
$V_{load}/V$ original two-terminal network, theory	0	1.10	1.15	1.69	2.31
$V_{load}/V$ Thevenin equivalent circuit, <del>theory</del> <sup>experiment</sup>	0	1.157	1.223	1.783	2.460
$V_{load}/V$ Thevenin equivalent circuit, theory	0	1.11	1.15	1.69	2.31

## 7. Load V-R Characteristic Plot

For each of these 2 circuits: The Original two-terminal Circuit and Thevenin Circuit, plot the load voltage vs. load resistance on the same plot. To create your plots you can use whichever software you would like (Excel, Matlab, etc), export your plot as an image and paste it in the appropriate place below. \_/8pt

Your plots should include:

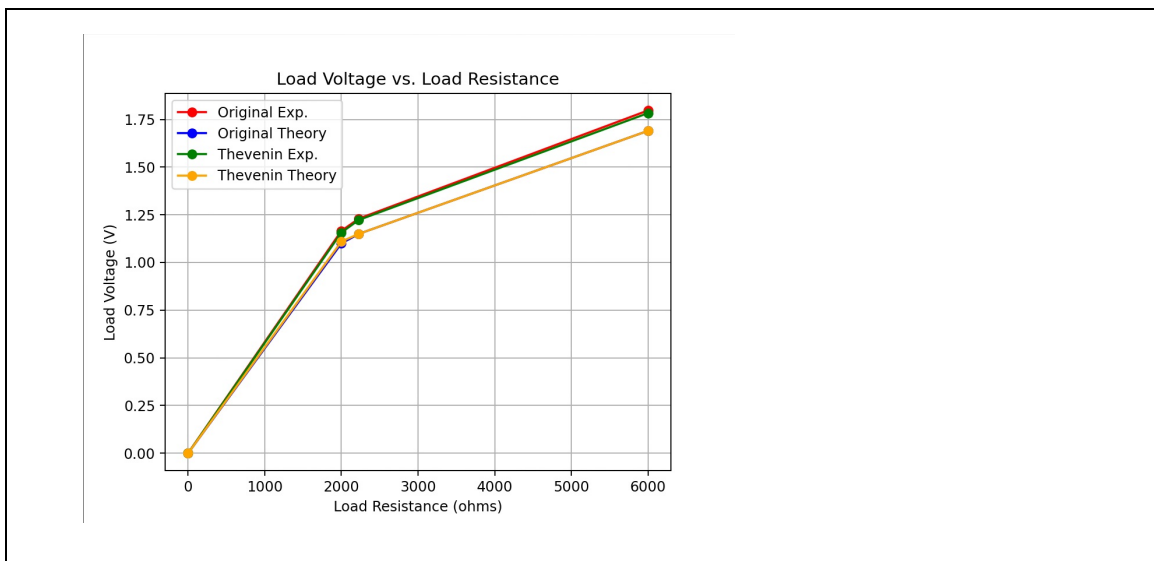- A Plot title
- Label your axes and show what unit of measure is used.
- Include a marking for your data-points.
- Include a line between your data-points in the same series.
- Include a legend.
- Make sure your scales are appropriate and visible.



5) Would you say original two-terminal network Circuit and Thevenin Circuit perform equivalently? Explain the reasons. \_/4pt

They perform equivalently.  
 From the figure above, the original two-terminal network circuit and Thevenin circuit show the same growth trend, where  $V_{oc}$  is the open-circuit voltage at the terminals  $V_{oc}$ , and  $R_o$  is the equivalent resistance at the terminals when the independent sources are all turned off.

Finally, before leaving lab, turn off all equipment and return cables to their proper place. Leave your lab station clean and ready for other students to use. Thank you!

TA check off: *Bang*