

# Lab3 Prelab Report

Name	杨润康	Score	
Stu NO.	2022533080		of 42

## Part One: Superposition Theorem

Consider the circuit given in Figure. 1, in which  $R_L$  is  $10k\Omega$

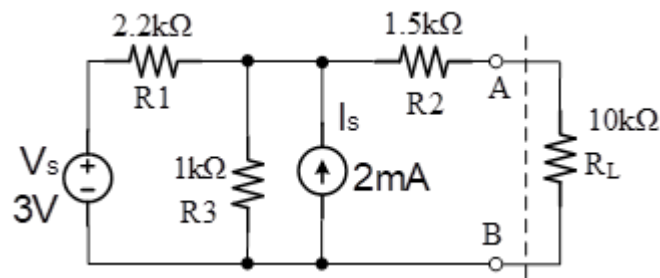


Figure 1.

Determine the  $U_L$  (voltage across  $R_L$ ) and  $I_L$  (current through  $R_L$ ) using superposition. \_\_\_/12pt

i. $U_s$ only	ii. $I_s$ only
<p><u>Equivalent Circuit</u></p> <p>KVL: <math>-3 + 2.2k i_1 + (i_2 - i_1) \times 1k = 0</math>  <math>1k \times (i_2 - i_1) + (1.5k + 10k) i_2 = 0</math>  <math>i_2 = I_L'</math>  <math>U_L' = 1.769V</math></p>	<p><u>Equivalent Circuit</u></p> <p>KCL: node 2: <math>2 \times 10^{-3} = \frac{V_2 - 0}{2.2k} + \frac{V_2 - 0}{1k} + \frac{V_2}{1.5k + 10k}</math>  <math>I_L' = \frac{V_2}{1.5k + 10k}</math>  <math>U_L' = 1.13V</math></p>
<p><math>U_L' = 1.769V</math></p> <p><math>I_L' = 76.9 \mu A</math></p>	<p><math>U_L'' = 1.13V</math></p> <p><math>I_L'' = 113 \mu A</math></p>
<p><math>U_L = 1.90V</math></p> <p><math>I_L = 190 \mu A</math></p>	

## Part Two: Thevenin's Theorem and Norton's Theorem

For the circuit given in Fig.2, remove  $R_L$  from the original circuit.

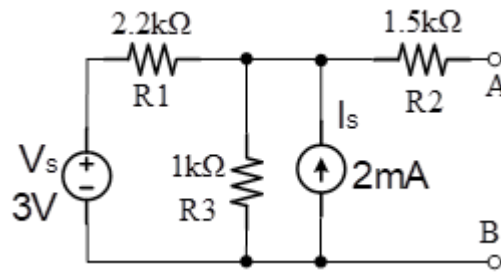


Fig. 2

1. Calculate the Thevenin's equivalent parameters following from the perspective of terminals A and B. Show all work. \_\_\_/9pt
  - a. open-circuit voltage  $U_{OC}$
  - b. short circuit current  $I_{sc}$
  - c. equivalent resistance  $R_0$

**a.**

Node 2, KCL:  $\frac{V_0 - V_1}{2.2k} + 2 \times 10^{-3} = \frac{V_1 - 0}{1k}$   
 $U_{oc} = U_{Th} = V_1 - 0$   
 $\Rightarrow U_{oc} = 2.31V$

**b.**



KCL:  $2 \times 10^{-3} + \frac{V_0 - V_1}{2.2k} = \frac{V_1 - 0}{1k} + \frac{V_1 - 0}{1.5k}$   
 $I_{sc} = \frac{V_1 - 0}{1.5k}$   
 $\Rightarrow I_{sc} = 1.06mA$

**c.**

$$R_0 = \frac{U_{oc}}{I_{sc}}$$

$$R_0 = 2.18k\Omega$$

2. Use your results to construct Thévenin and Norton Equivalent Circuit. \_\_\_/7pt

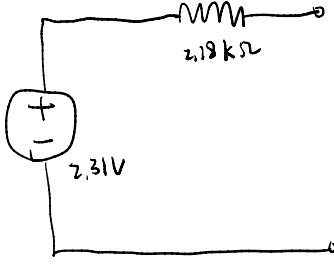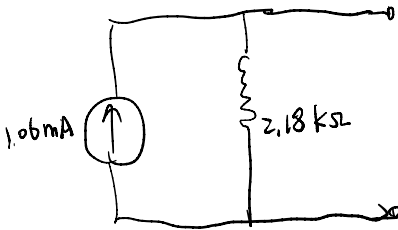
Thévenin Equivalent Circuit	Norton Equivalent Circuit
	

### 3. Validate Thevenin theorem.

#### 1) Calculate the external characteristics of the linear two-terminal active network

As shown in Fig.3, the variable resistor  $R_L$  is connected between terminals A and B of the two-terminal active network. Change the resistance of  $R_L$ , as shown in Table1, and measure the external characteristics of the network. Record the corresponding voltages and currents into Table1. \_\_/6pt

Fig.3

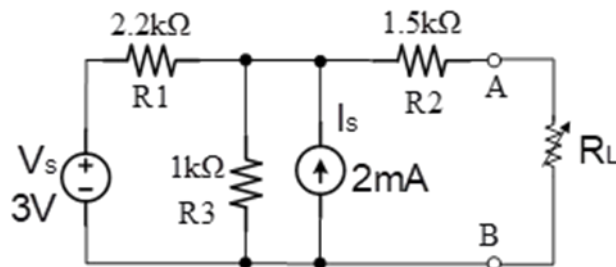

#### 2) Calculate the external characteristics of the Thévenin Equivalent Circuit

According to your Thévenin Equivalent Circuit in step2, a variable resistor  $R_L$  is used as load.

Calculate the external characteristics of the Thévenin Equivalent Circuit. Record the corresponding voltages and currents into the Table 1. \_\_/14pt

Table 1.

$R_L/\Omega$	0	1k	2k	$R_0$	6k	12k	$\infty$
$U_L/V$ Fig.8 original two-terminal network	0	$725 \times 10^{-3}$	1.10	1.15	1.69	1.96	2.31
$U_L/V$ Thevening equivalent circuit	0	$726 \times 10^{-3}$	1.11	1.15	1.69	1.95	2.31
$I_L/mA$ Fig.8 original two-terminal network	-1.06	$-725 \times 10^{-3}$	$-552 \times 10^{-3}$	$-529 \times 10^{-3}$	$-282 \times 10^{-3}$	$-163 \times 10^{-3}$	$-2.31 \times 10^{-6}$
$I_L/mA$ Thevening equivalent circuit	-1.06	$-726 \times 10^{-3}$	$-553 \times 10^{-3}$	$-530 \times 10^{-3}$	$-282 \times 10^{-3}$	$-163 \times 10^{-3}$	0